
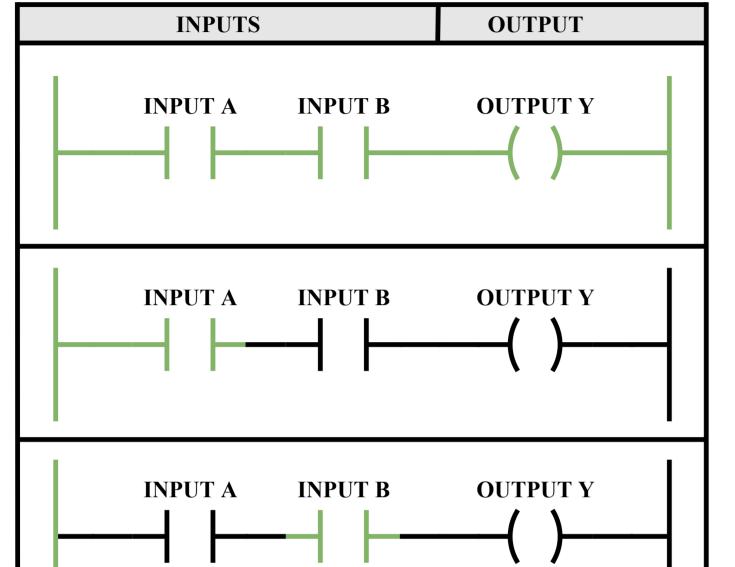



BUTTON A	BUTTON B	LIGHT
true	true	true
true	false	false
false	true	false
false	false	false

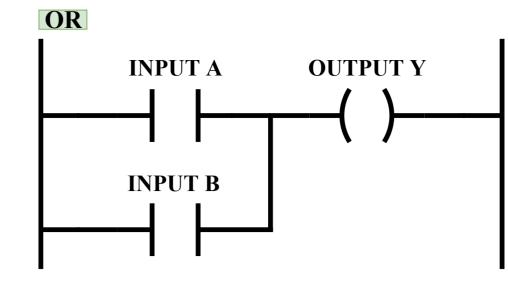


INPUT A INPUT B OUTPUT Y




INP	OUTPUT	
A	В	Y
true	true	true
true	false	true
false	true	true
false	false	false

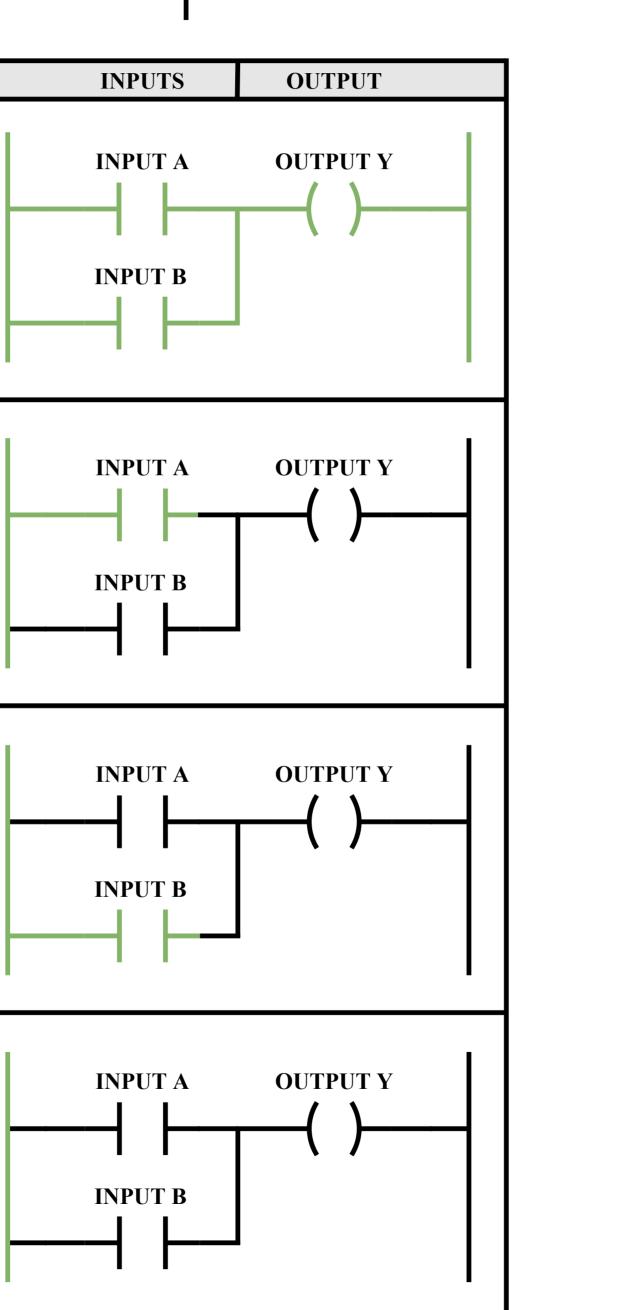


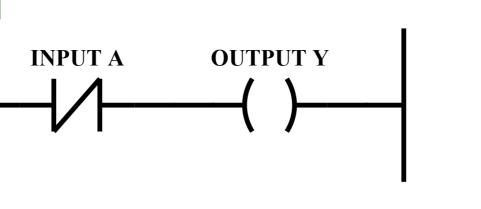

PUT	OUTPUT		INPUT	OUTPUT	
A	Y	▎┌		-	_
ue	false		INPUT A	OUTPUT Y	
lse	true	11	<u> </u>	(_
			INPUT A	OUTPUT Y	-

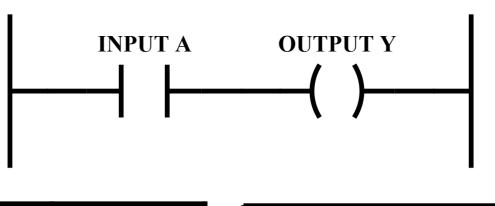

INPUT	OUTPUT
INPUT A	OUTPUT Y
INPUT A	OUTPUT Y

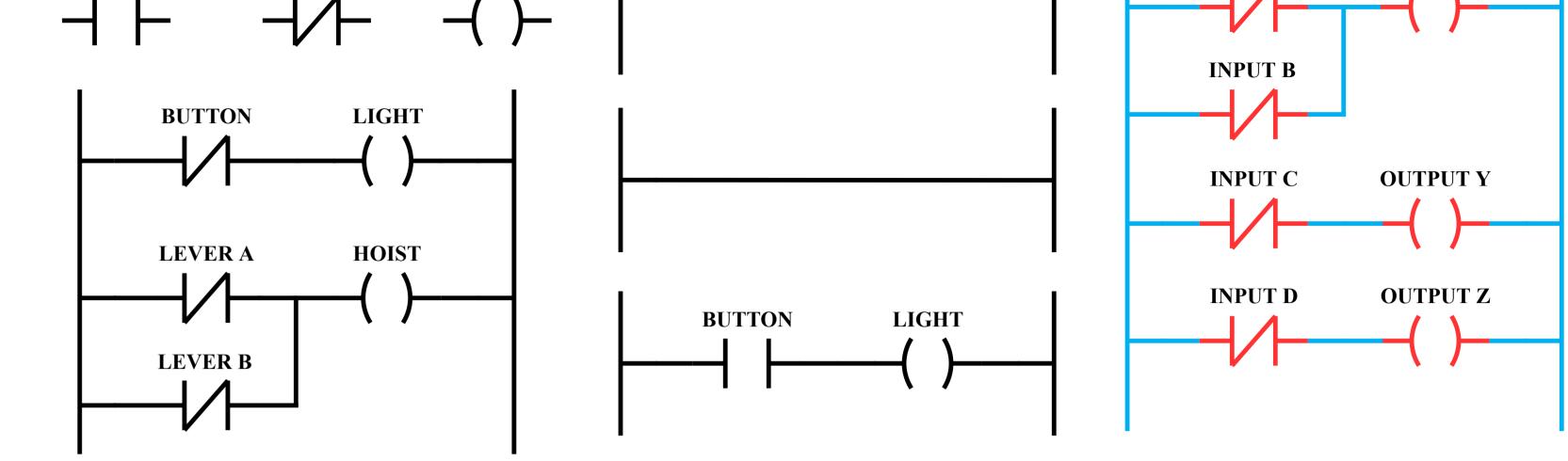

INPUT A OUTPUT X

NORMALLY NORMALLY
OPEN CONTACT CLOSED CONTACT COIL